

Unit IV

Programmable Logic Devices

by
Prof. Sujata Wakchaure

Introduction

- To design a circuit, designer can select most appropriate IC from the available ICs for the circuit
- The design may have to be modified to meet the special requirements of these devices
- **Advantages of design method (which uses Fixed Function IC):**
 - Low development
 - Fast turn around of design
 - Relatively easy to test the circuit
- **Disadvantages of design method (which uses Fixed Function IC)**
 - Large board space requirement
 - Large power requirement
 - Lack of security
 - Additional cost, space, power requirement, etc.

Introduction (Contd..)

- **ASIC (Application Specific Integrated Circuit)**
- **Advantages of ASIC :**
 - Reduced space requirement
 - Reduced power requirement
 - Design implemented in this form are almost impossible to copy
 - Low Cost
- **Disadvantages of ASIC :**
 - Initial development cost may be enormous
 - Testing methods may have to be developed

Programmable Logic Devices (PLD)

- Special purpose ICs
- It is user configurable and is capable of implementing logic functions
- PLDs can be programmed as per requirement
- It is a VLSI chip

PLDs (Contd..)

- The purpose of a PLD device is to permit elaborate digital logic designs to be implemented by the user in a single device
- PLDs Can be erased electrically and reprogrammed with a new design
- **Advantages of fixed function ICs :**
 - Short design cycle
 - Low development cost


PLDs (Contd..)

- **Advantages over Fixed function ICs :**
 - Reduction in board space requirement
 - Reduction in power requirement
 - Design security
 - Compact circuitry
 - Higher switching speed
- **Advantages of ASIC :**
 - High densities
 - Low quantity production cost
 - Reduced space requirement

PLDs (Contd..)

- **The Architecture and various other features of PLDs are:**
 - ROM
 - Programmable Logic Arrays (PLA)
 - Programmable Array Logic (PAL)
 - Simple Programmable Logic Devices (SPLDs)
 - Complex Programmable Logic Devices (CPLDs)
 - Field Programmable Gate Arrays (FPGA)

Types of PLDs (Cont.)

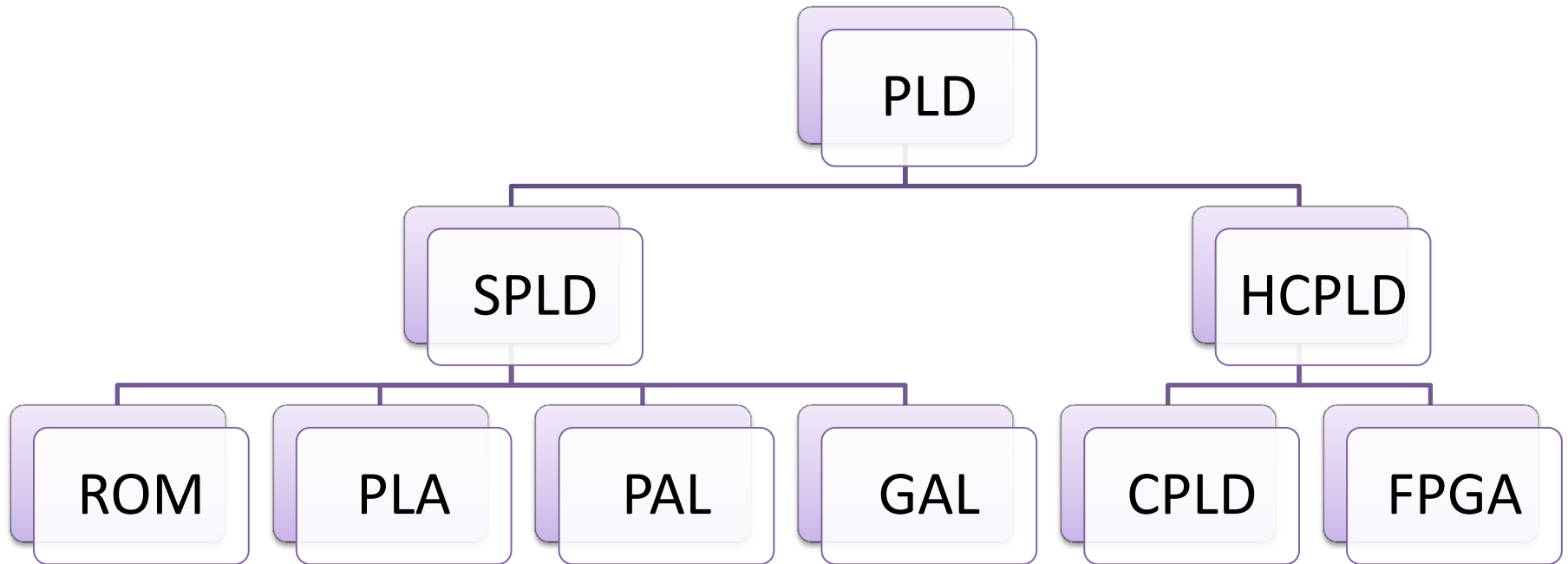

PLDs (Contd..)

- The differences between the first three categories are these:
 1. **ROM:** In a ROM, the input connection matrix is hardwired. The user can modify the output connection matrix.
 2. **PAL:** In a PAL / GAL (Generic Array Logic) the output connection matrix is hardwired. The user can modify the input connection matrix.
 3. **PLA:** In a PLA the user can modify both the input connection matrix and the output connection matrix.

| Device | AND-array | OR-array |
|--------|--------------|--------------|
| PROM | Fixed | Programmable |
| PLA | Programmable | Programmable |
| PAL | Programmable | Fixed |
| GAL | Programmable | Fixed |

ROM as PLD

- ROM is basically a combinational circuit which has n I/Ps & m O/Ps
- A ROM size $M \times N$ has M number of locations and N no. of bits can be stored at each location


 


Fig 1: ROM as a Combinational Circuit


ROM as PLD (Contd..)

 

E.g.

1. $W = m_0 + m_1 + m_3 + m_7$
2. $X = m_2 + m_4 + m_6 + m_7$
3. $Y = m_3 + m_5 + m_6$
4. $Z = m_2 + m_5 + m_7$

ROM as PLD (Contd..)

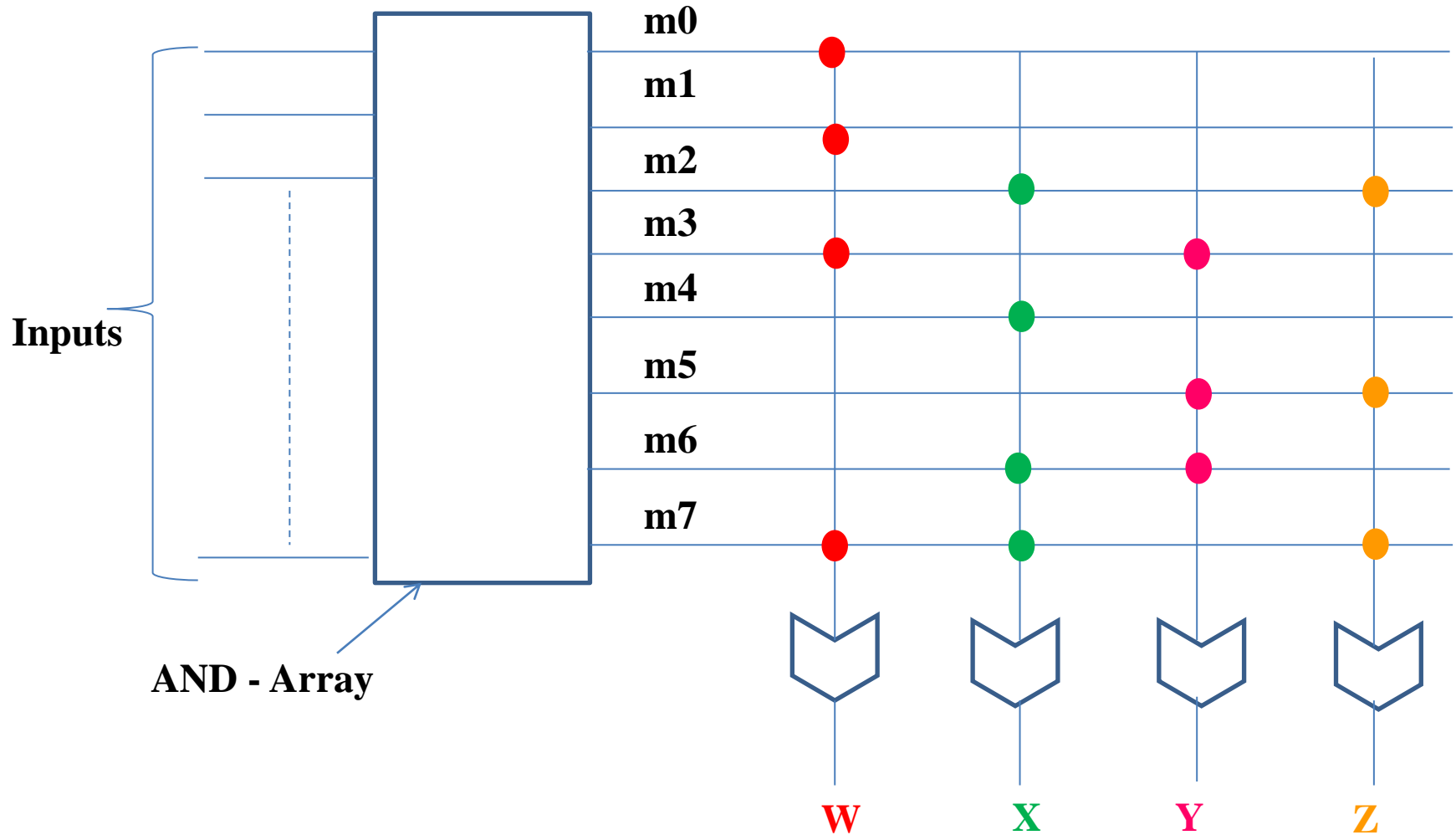


ROM as PLD (Contd..)

- **Advantages of using ROM as a PLD:**
 - Ease of design
 - Design can be changed or modified rapidly
 - It is usually a faster circuit
 - Cost is reduced
- **Disadvantages:**
 - Increased power requirement
 - Enormous increase in size

Programmable Logic Array (PLA)

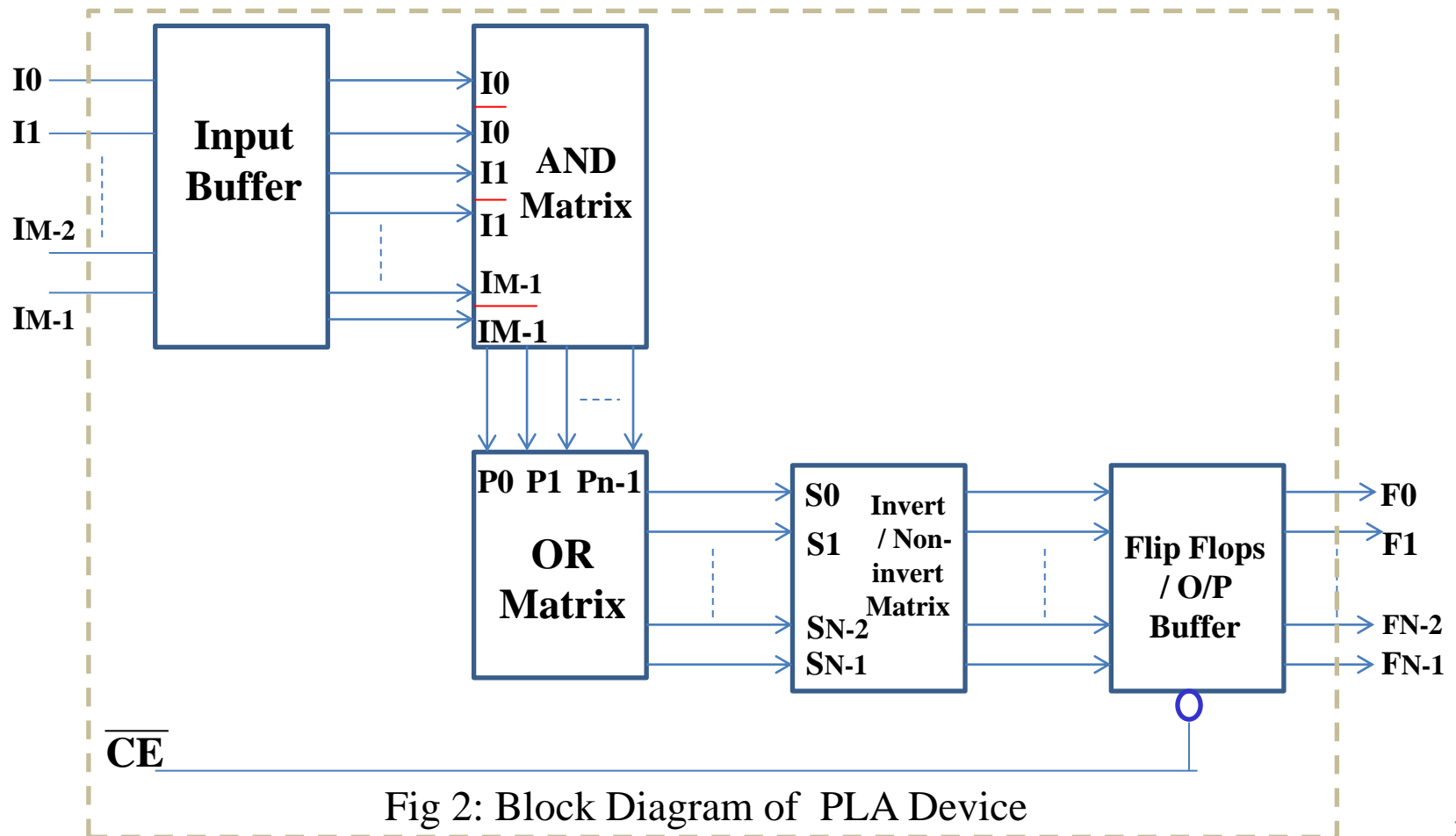
- It is a type of fixed architecture logic device with programmable AND gates followed by programmable OR gates




PLA (Contd..)

 1. Input Buffer :

- Inputs are required to limit loading of sources



(a)

 

(b)

PLA (Contd..)

2. AND Matrix :

- It IS USED TO FORM Product terms
- $P = I_0.\overline{I_0} + I_1.\overline{I_1} + \dots + I_{M-1}.\overline{I_{M-1}}$

3. OR Matrix :

- It is used to produce the logical sum of product term O/P of AND Matrix
- $S_0 = P_0 + P_1 + \dots + P_{n-1}$

PLA (Contd..)

4. Invert / Non-Invert Matrix:

- This is programmable buffer that can be set for inverting & non inverting operations corresponding to active-low or active high O/P respectively
- E.g. In case of EX-OR gate, if the fuse is not damage (intact), the O/P is S and if fuse is damaged O/P is \overline{S}
- In Fig b S or \overline{S} depending upon whether the fuse is intact or open

 


Fig (a)

 


Fig (b)

PLA (Contd..)

- Example:

| A | B | C | Y1 | Y2 |
|---|---|---|----|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

PLA (Contd..)

- **Step1:** To make truth table or observe truth table
- **Step 2:** Find out the minimal SOP form for given function (i.e. for Y1 & Y2)





$$Y1 = A\overline{B}\overline{C} + A\overline{B}C + ABC$$

$$Y1 = A\overline{B} + AC$$

$$Y2 = BC + AC$$

PLA (Contd..)

    - **Step 3: Find out no. of I/P Buffer**
 - What is I/P Buffer ?



No. of I/P Buffer = No. of Variables

No. of I/P Buffer = 3

PLA (Contd..)

- **Step 4:** Find out the no. of programmable AND gate


No. of programmable AND Gate = No. of Minterms

**** No. of Minterms should not be repeated**

$$\begin{array}{cc} 1 & 2 \\ Y1 = AB + AC \\ 3 & 4 \\ Y2 = BC + AC \end{array}$$

No. of programmable AND Gate = 3 (Because AC is repeated)

PLA (Contd..)

 


PLA (Contd..)

- **Step 5:**

Find out the no. of programmable OR gate

$$\begin{aligned}\text{No. of programmable OR Gate} &= \text{No. of Functions} \\ &= 2 \text{ (Y1 \& Y2)}\end{aligned}$$

PLA (Contd..)

 


PLA Realization of Functions

$$F_1 = a'bd + abd + ab'c' + b'c$$

$$F_2 = c + a'bd$$

$$F_3 = bc + ab'c' + abd$$

| <i>a</i> | <i>b</i> | <i>c</i> | <i>d</i> | <i>f</i> ₁ | <i>f</i> ₂ | <i>f</i> ₃ |
|----------|----------|----------|----------|-----------------------|-----------------------|-----------------------|
| 0 | 1 | – | 1 | 1 | 1 | 0 |
| 1 | 1 | – | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | – | 1 | 0 | 1 |
| – | 0 | 1 | – | 1 | 0 | 0 |
| – | – | 1 | – | 0 | 1 | 0 |
| – | 1 | 1 | – | 0 | 0 | 1 |

 

PLA (Contd..)

- **H.W.**

1. **Binary to Gray**


2. **$F1(A,B,C)=\sum m(4,5,7)$**

$F2(A,B,C)=\sum m(3,5,7)$


Programmable Array Logic (PAL)

- A most commonly used type of PLD
- It have fixed OR array
- Advantage of Fixed OR array is Simplicity
- Disadvantage is Flexibility

PAL (Contd..)

 

PAL (Contd..)

 


PAL (Contd..)

- Example

$$\begin{aligned} 1. \quad X(A,B,C) &= \sum m(2,3,5,7) &= \overline{A}B + \overline{A}C \\ 2. \quad Y(A,B,C) &= \sum m(0,1,5) &= \overline{A}\overline{B} + \overline{A}B \\ 3. \quad Z(A,B,C) &= \sum m(0,2,3,5) &= \overline{A}\overline{B} + \overline{A}C + \overline{A}BC \end{aligned}$$

- Step 1: See the Minterms
- Step 2: Minimize expression using K-Map
- Step 3: Look at the variable i.e. 3. So 3 I/P buffers required
- Step 4: No. of AND arrays
- Step 5: No. of OR gates

PAL (Contd..)

 


Implementation of 4:1 MUX using PAL

| Select inputs | | Outputs |
|---------------|----|---------|
| S1 | S0 | Y |
| 0 | 0 | D0 |
| 0 | 1 | D1 |
| 1 | 0 | D2 |
| 1 | 1 | D3 |

$$Y = \bar{S}_1\bar{S}_0D_0 + \bar{S}_1S_0D_1 + S_1\bar{S}_0D_2 + S_1S_0D_3$$

4:1 MUX (Contd..)

 

PAL (Contd..)

- **Examples**

1. **BCD to Excess-3**

2. **$F1(A,B,C) = \sum m(0,1,5,6,7)$**

Difference between PROM, PLA & PAL

| PROM | PLA | PAL |
|---|--|--|
| It is cheap and easy to use | It is expensive than PAL and PROM and complicated to use | Moderately expensive and moderately complicated |
| There are fixed AND arrays and programmable OR arrays | AND arrays and OR arrays Are programmable | Only the AND array is programmable. Or array is fixed |
| SOP function in standard form only can be implemented | Any SOP function can be implemented | Any SOP function can be implemented |
| It is possible to decode any minterm | We can get any desired minterm by programming the AND matrix | We can get any desired minterm by programming the AND matrix |

FPGA

- FPGA : Field Programmable Gate Arrays
- FPGA is a IC which is used to increase the effective size and to add more functionality in a single programmable device
- FPGAs are configurable and programmable
- Programmable components of FPGA
 1. Logic Blocks
 2. Interconnects

FPGA (Contd..)


- What is the term “**Field**” programmable?
 - Field stands for programming in the field.
- **FPGA generally contains**
 - PLDs
 - Logic gates
 - RAM
 - Other H/W components
- **Family of FPGA**
 - Xilinx
 - Actel
 - Altera

FPGA (Contd..)

- **Advantages of FPGA**
 - Inexpensive
 - Easy to realize
 - Less Design and Testing time


FPGA (Contd..)

- **Basic Architecture of FPGA**

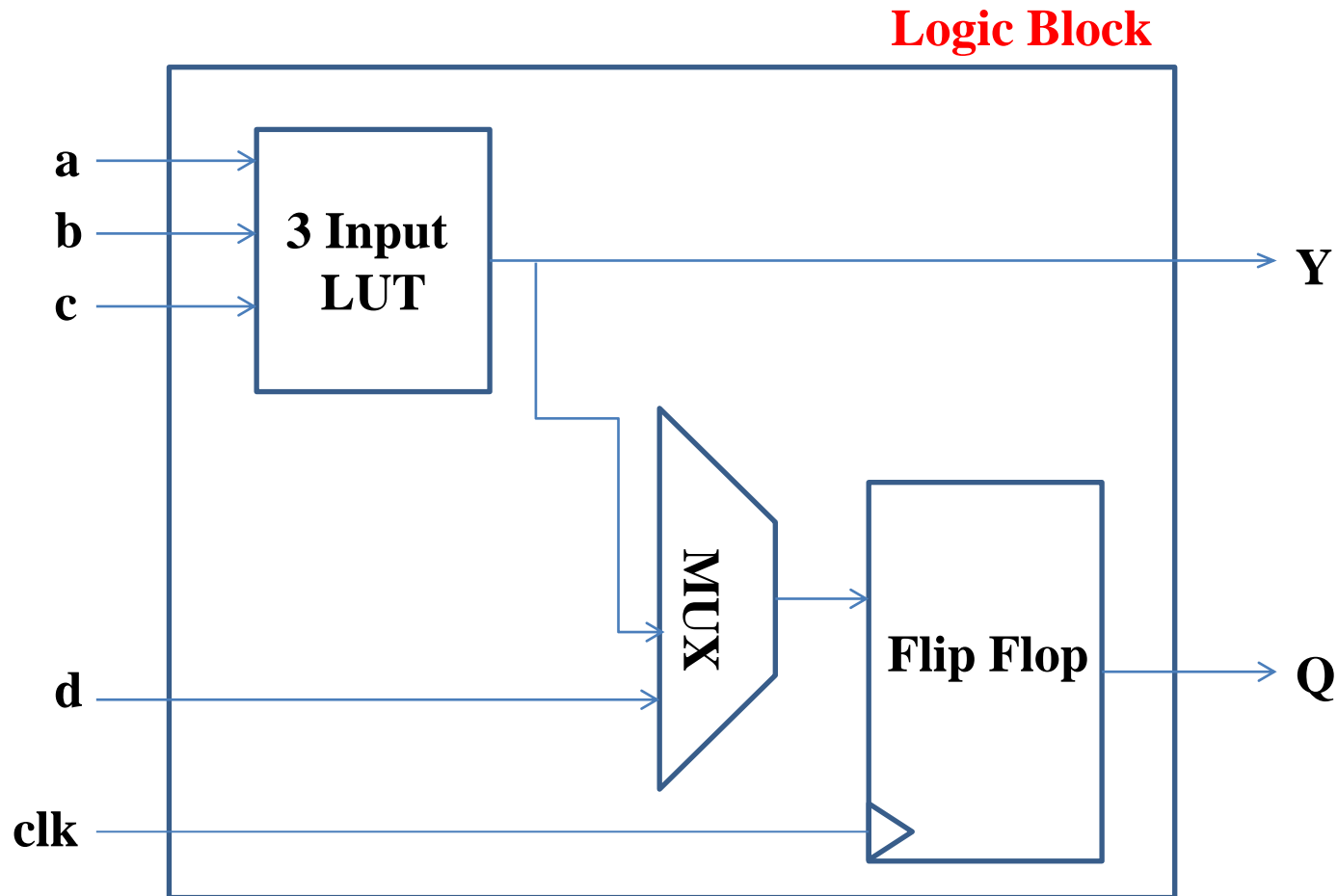


FPGA (Contd..)

 - **What does the Logic Block contains in FPGA ?**
 - Logic block of FPGA contains LUT (Look Up Table)
- **What is LUT?**
 - E.g. $Y = (a \& b) \mid !c$




FPGA (Contd..)

| a | b | c | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 

Architecture of FPGA

 

Architecture of FPGA (Contd..)

- The basic architecture consist of array of configurable logic blocks
- **Logic blocks:**
 - Connected to the I/O blocks through common row/column programmable interconnects
 - The common row/column interconnects are known as Global interconnects