

# **Ring Counters and Johnson's Ring Counter**


by

Prof. Sujata Wakchaure

# Ring Counter


- It is a sequential logic ckt that is constructed using shift register
- Same data recirculates in the counter depending on the clock pulse
- It is self decoding ckt
- The O/P of last shift register is fed to the input of the 1<sup>st</sup> register

# Ring Counter (Contd..)

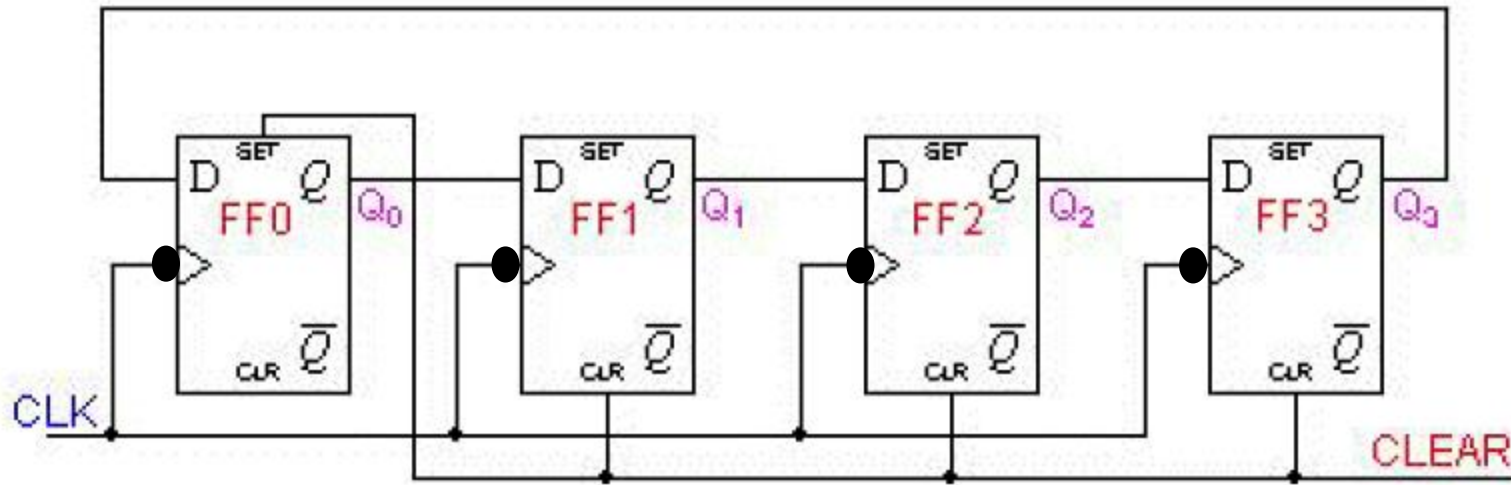


- For Normal Counter
  - » No. of states =  $2^n = 2^4 = 16$
  - » Max Count =  $2^n - 1 = 16 - 1 = 15$
- For Ring Counter
  - » No. of States = No. of FF used

# Ring Counter (Contd..)


- Ring counter is Synchronous counter and we have used Overriding I/Ps (ORI)
- ORI => Preset(PR) and Clear(CLR)
- If PR = 0 then Q = 1  **It will set FF**
- If CLR = 0 then Q = 0
- Why PR & CLR are called as ORI?
- For FF-1, 2, & 3 ORI is connected to CLR & for FF-0 it is connected to PR
- Therefore,  $\left. \begin{array}{l} Q1=0 \\ Q2=0 \\ Q3=0 \end{array} \right\} \text{Because CLR}=0$   
**Q0=1 => Because PR=0**

# Ring Counter (Contd..)

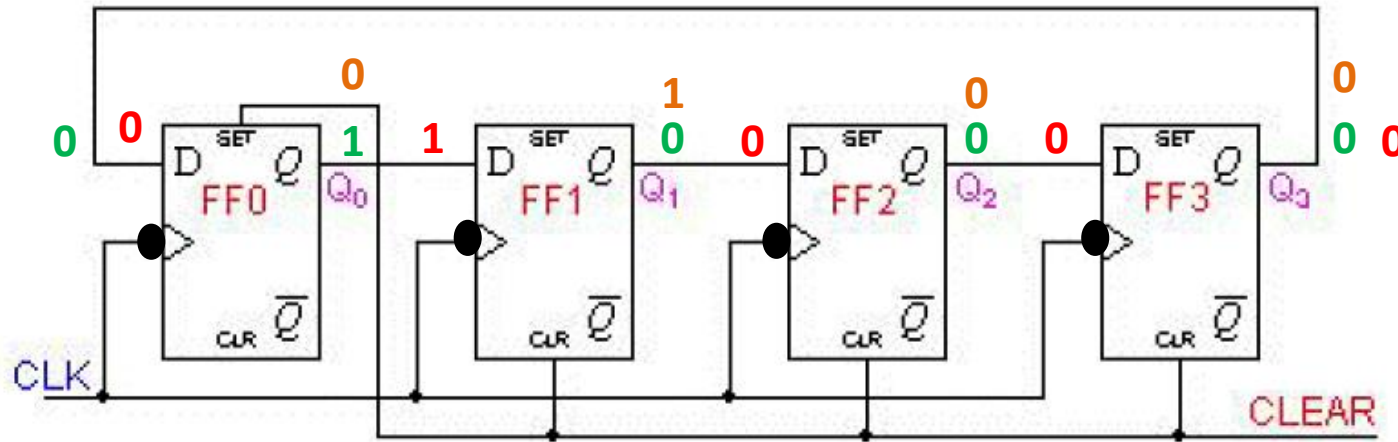


ORI	CLK	Q0	Q1	Q2	Q3
	X	1	0	0	0
1	↓	0	1	0	0
1	↓				
1	↓				
1	↓				

# Ring Counter (Contd..)

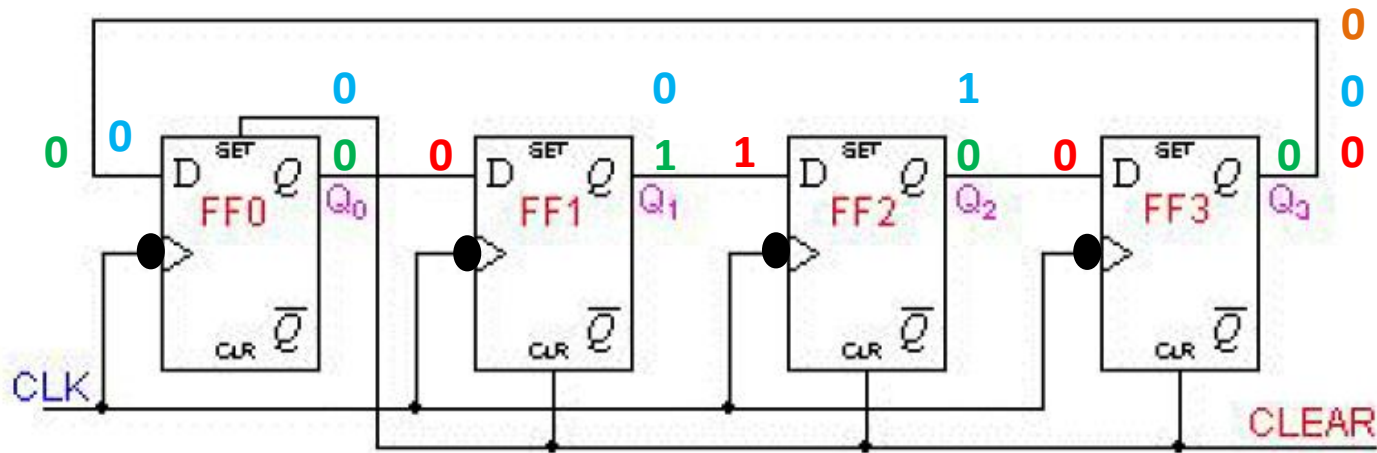

ORI	CLK	Q0	Q1	Q2	Q3
	X	1	0	0	0
1	↓	0	1	0	0
1	↓	0	0	1	0
1	↓	0	0	0	1
1	↓	1	0	0	0

# Ring Counter (Contd..)

 


# Johnson's Ring Counter

- Also known as **Twisted / Switch Tail Ring Counter**
- It is modified Ring Counter, where the inverted O/P from the last FF is connected to the I/P to the first FF
- If we compare Ring Counter and Johnson's Ring Counter then Johnson's Ring Counter is much more better than Ring Counter.
- There are 2 changes in Johnson's Ring Counter:
  1. The shifting to the CLR I/P than the Preset I/P
  2. Q3 is connected to the D0




# Johnson's Ring Counter (Contd..)

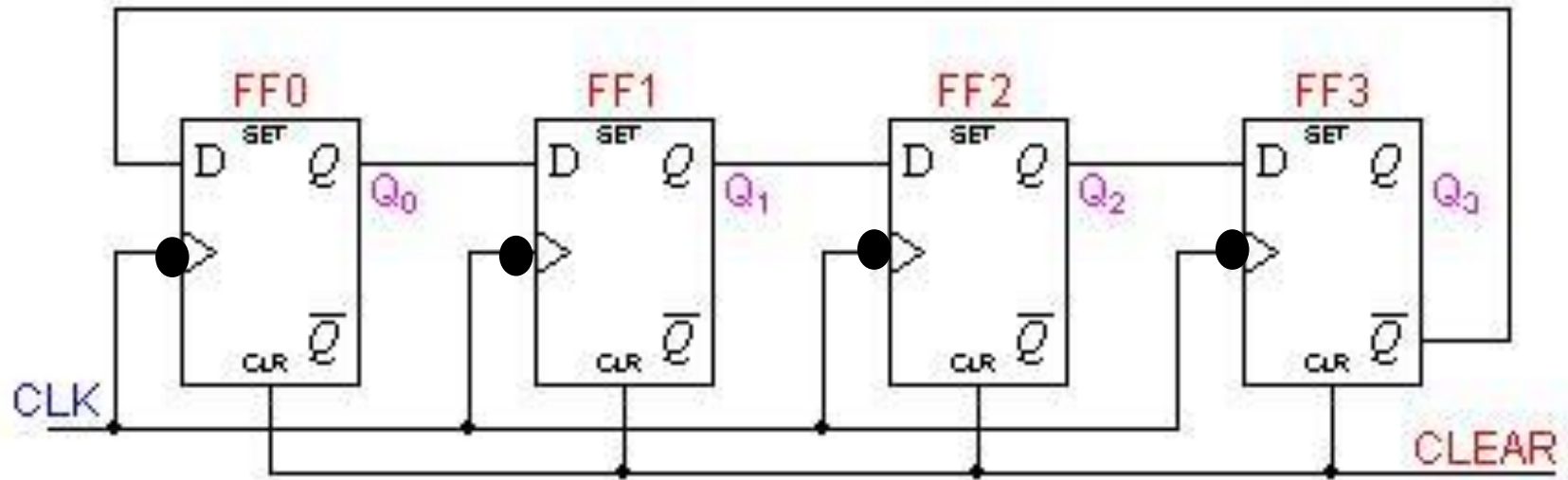


- Initially when ORI I/P is low, the O/P  $Q_0=Q_1=Q_2=Q_3=0$

# Johnson's Ring Counter (Contd..)

CLR	CLK	Q0	Q1	Q2	Q3
	X	0	0	0	0
1	↓	1	0	0	0
1	↓	1	1	0	0
1	↓	1	1	1	0
1	↓	1	1	1	1
1	↓	0	1	1	1
1	↓	0	0	1	1
1	↓	0	0	0	1
1	↓	0	0	0	0

**No. of States = 2 x No. of FF**

# Johnson's Ring Counter (Contd..)

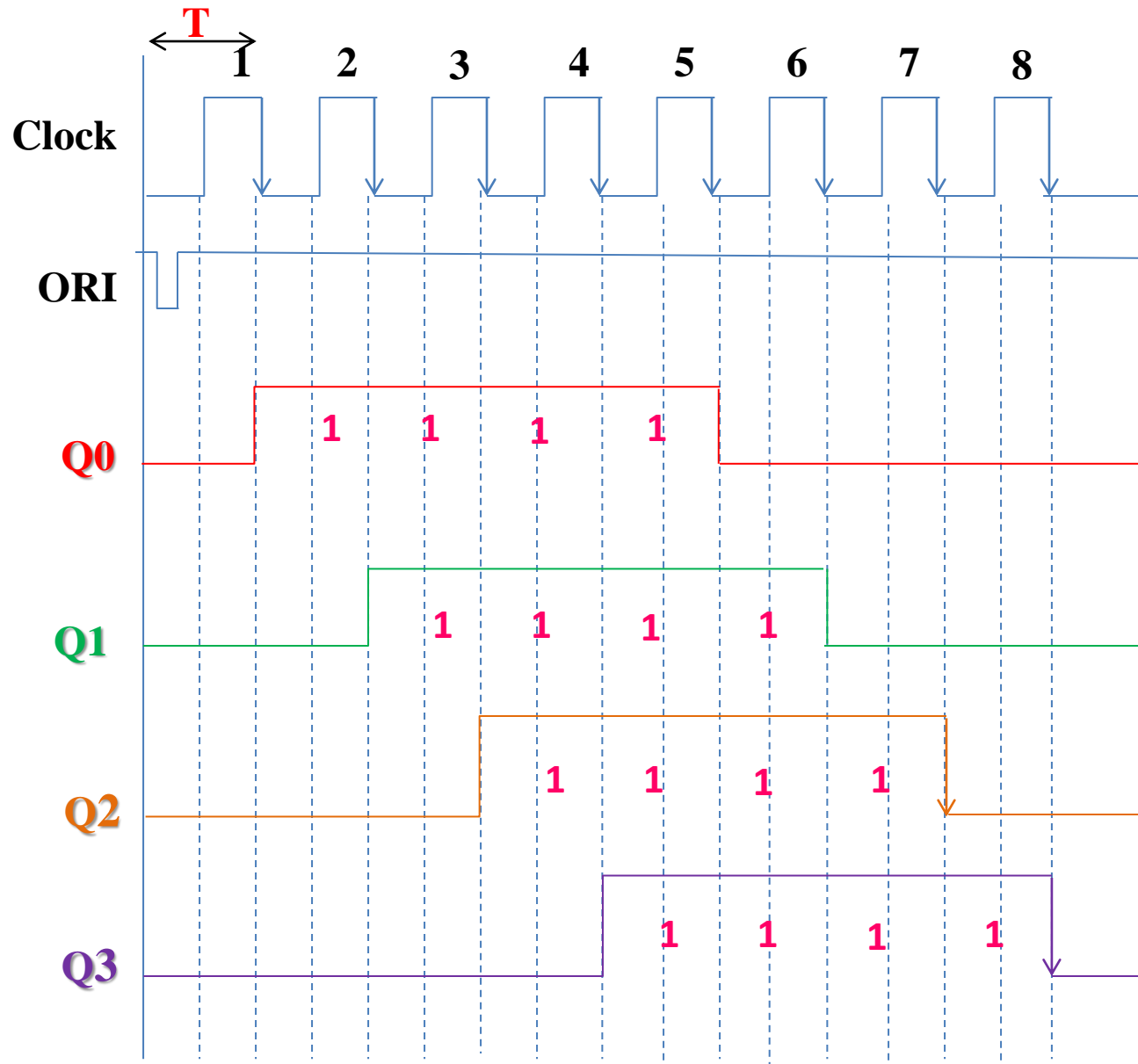

# BCD Counter

- It is a special type of counter which can count to ten on the applications of a clock signal
- **Negative Edge Triggered**
  - $Q$  is Clock  $\Rightarrow$  Up Counter
- **Negative Edge Triggered**
  - $\overline{Q}$  is Clock  $\Rightarrow$  Down Counter
- **Positive Edge Triggered**
  - $\overline{Q}$  is Clock  $\Rightarrow$  Up Counter
- **Positive Edge Triggered**
  - $Q$  is Clock  $\Rightarrow$  Down Counter

# Cascading of Counters

- What if I have 2 counters?




- After cascading the resulting FF:




# BCD Counter (Contd..)

- No. of States = 10

 
 
# BCD Counter (Contd..)

- As we have 4 bit our counting will start from 0000 to 1111
- But we want to stop it at 1001 because this is BCD Counter
- So what we can do?



- We have to Convert 4 bit asynchronous Up Counter to Decade Counter


# BCD Counter (Contd..)

- To achieve this conversion we need to focus on 1010 state
- As soon as 1010 has arrived, we have to reset our FF by using 2 asynchronous I/Ps i.e. PR and CLR

PR = 0    O/P = 1 ← SET

CLR = 0    O/P = 0 ← RESET

 
- We have to use NAND gate to achieve this





# BCD Counter (Contd..)

Logic 1

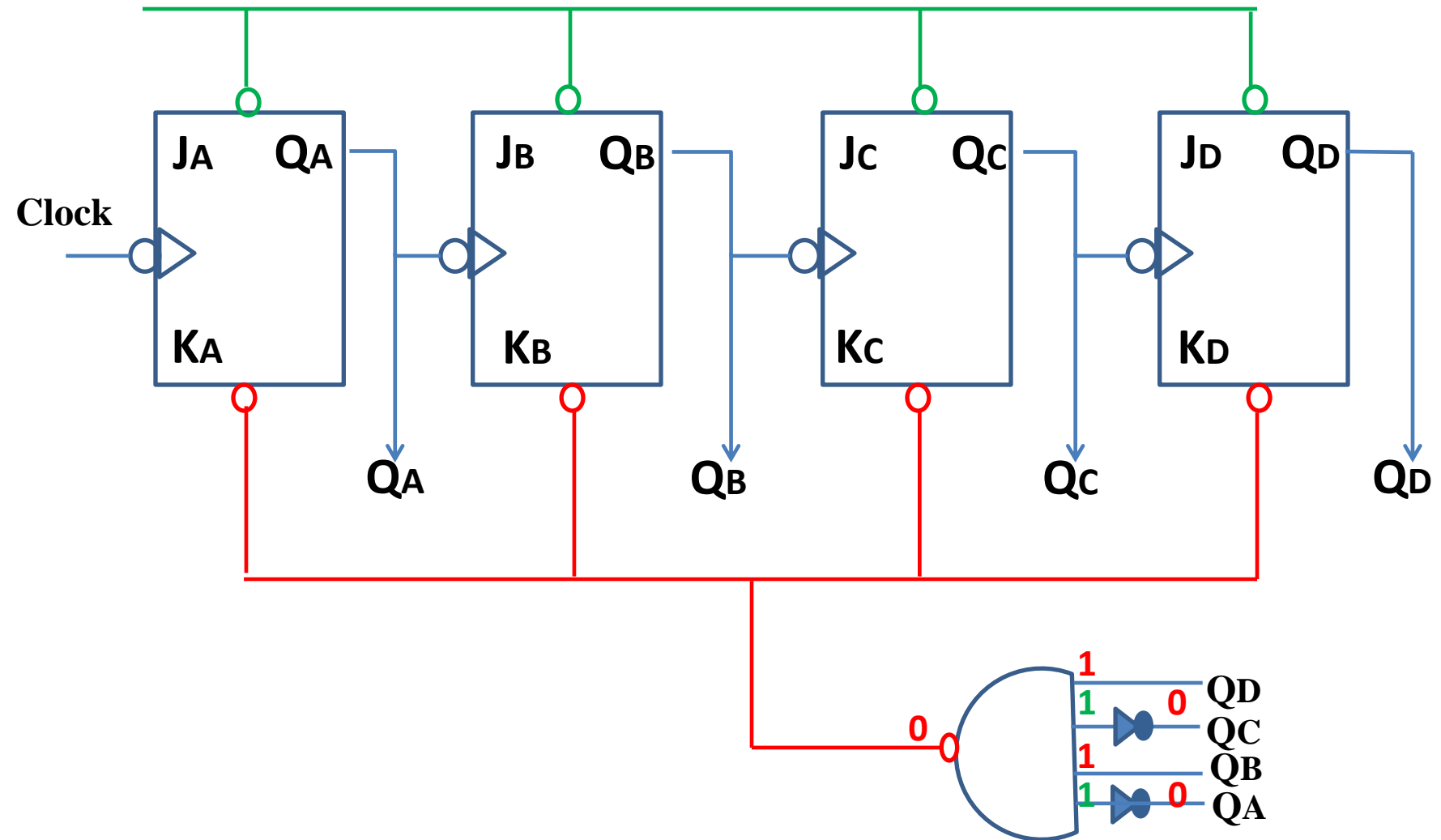

# Modulus of Counter (IC 7490)

- **2 – Bit** Ripple Counter is called as **MOD - 4** Counter or **Modulus 4** Counter
- **3 – Bit** Ripple Counter is called as **MOD – 8** Counter or **Modulus 8** Counter

$n = \text{No. of bits}$

$\text{State / MOD No.} = 2^n$


$\text{Modulus of Counter} = \text{No. of States}$

# MOD -6 Counter Using MOD 8 Counter

- MOD – 6 Counter
- MOD – 8 Counter

MOD -6 Counter :

000  
001  
010  
011  
100  
101

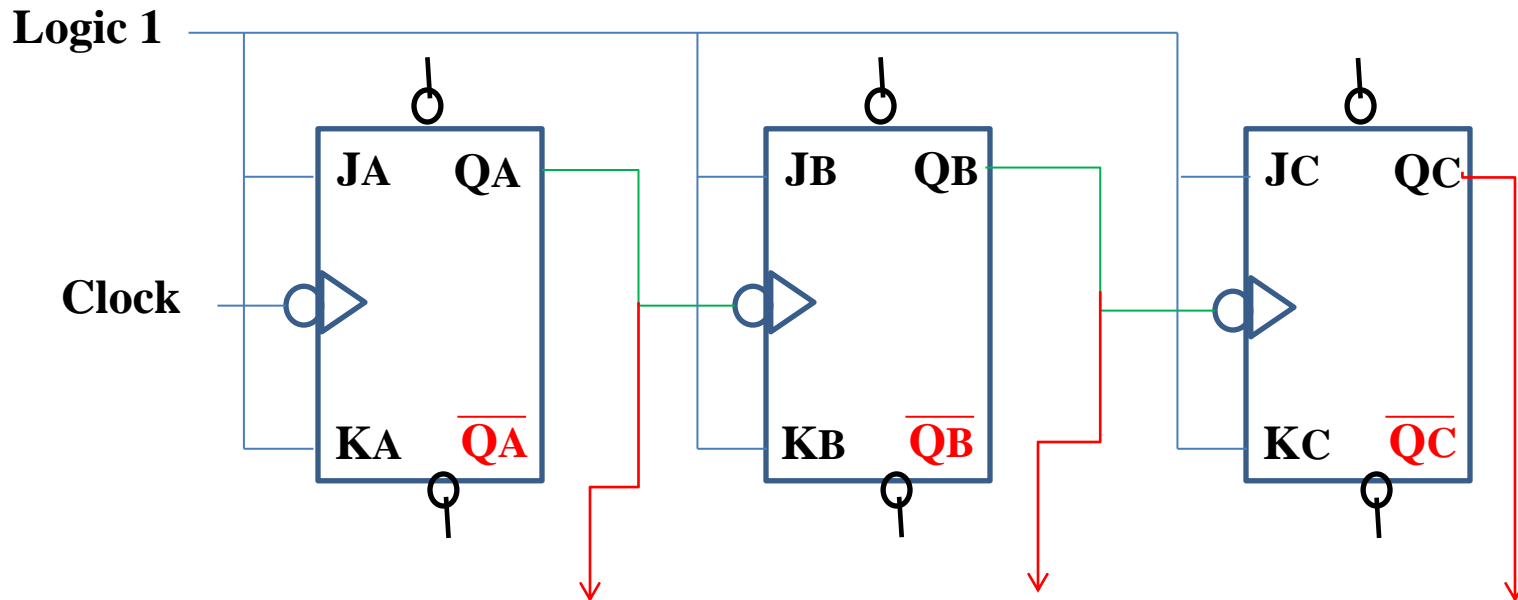

# MOD -6 Counter Using MOD 8 Counter (Contd..)

- If  $PR = 0$   $O/P = 1$
- If  $CLR = 0$   $O/P = 0$
- Now in what way we can use this PR & CLR I/Ps to count up to 5 instead of 7?

