

# **Sequence Detector & Generator**

by

Prof. Sujata Wakchaure

# Sequence Detector

- In digital electronics a movement of data is commonly called as a “**Bit Stream**”
- Any one bit in a bit stream looks identical to many other bits
- It is imp for receiver to identify beginning & ending of a message
- This is a job of special bit sequence called **Flags**
- A flag is simply a bit sequence that serves as a marker in the bit stream
- To **detect a flag** in a bit stream a **Sequence Detector** is used

# Sequence Detector (Contd..)

- The stream of bit has been feed as I/P, when clock is high & particular Pattern / Sequence is detected
- As soon as a sequence is detected, the O/P becomes high & then again becomes low



# Sequence Detector (Contd..)

- Lets  $X = 0110010100\dots$
- In this I/P Bit stream I want to detect 010
- We have 2 possibilities here
  1. When we consider overlapping
  2. When we do not consider the overlapping

**0110010100**



**010**

**O/P Y = 0**

**0110010100**



**010**

**Y = 00**

# Sequence Detector (Contd..)

0110010100



**010** Y = 000


0110010100



**010** Y = 000000

– Now there is overlapping

0110010100

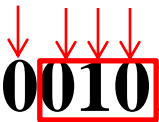

**Y = 0000001**

0110010100



**Here Pointer is not only at 1 But at 01**

**Final Output Y = 00000010010....**

# Sequence Detector (Contd..)


**0110010100**

- **Step 1:** Obtain the state diagram (Consider Mealy m/c)
  - Starting state of detection = S0
  - When pointer is at S0 = The 1<sup>st</sup> bit is **0**
  - When there is 0 = pointer will point to next state

S0= Reset

S1 = 0

S2= 01

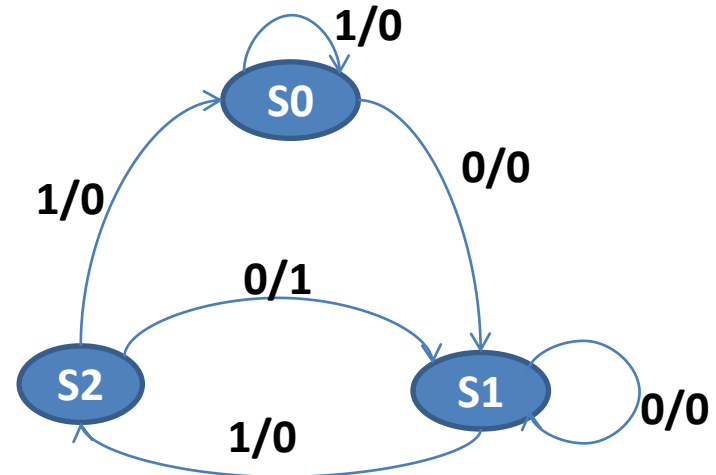


# Sequence Detector (Contd..)

- **0110010100**
  - Now Pointer is on **S0** =>
    - If I/P = **1** , O/P= 0 (Reset State)
  - Now if Pointer is on **S1** =>
    - If Next Bit or I/P = **0** , O/P = 0 (Reset State)
    - If I/P = **1** then, got to next State =S2 , O/P = 0
  - Now if Pointer is on **S2** =>
    - If Next Bit or I/P = **0** , then go to S1, O/P = **1** (Reset State)
    - Because sequence **010** is detected here
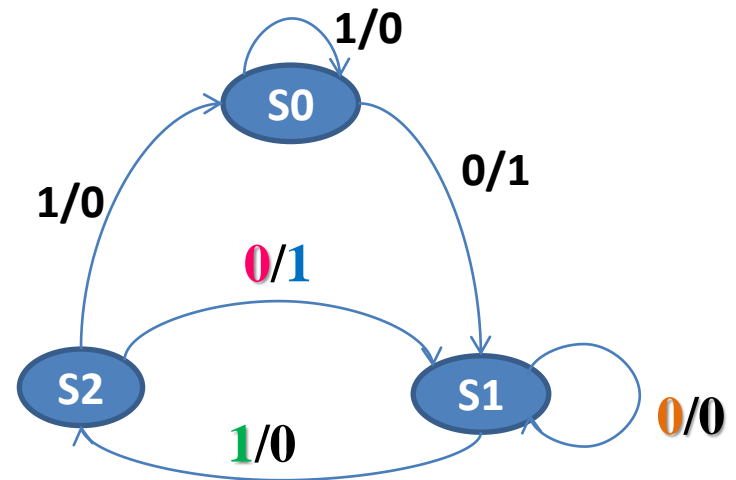
# Sequence Detector (Contd..)

0110010100

- Currently pointer is at S1 with O/P = 1
- Next bit is 1, then again pointer will go to S2
- And the next bit is 0
- Then again O/P = 1 (010)





# Sequence Detector Example

- Design a sequence detector to detect 3 or more consecutive 1s in a string of bits coming through an I/P line
- If  $X = 00\boxed{111}0\boxed{111}10\dots$   
     $Y = 0000\textcolor{red}{1}000\textcolor{red}{1}\textcolor{green}{1}0 \longleftrightarrow (\text{Overlapping})$   
     $Y = 00001000100 \longleftrightarrow (\text{Non - Overlapping})$

# Sequence Detector Example (Contd..)

- **Step 1: State Diagram**


S0=Reset

S1= 1

States	Has	Awaits
S0= Reset	.....	111.....
S1=1	1	11.....
S2=11	11	1
S3=111	111	.... / 0

# Sequence Detector Example (Contd..)

- **Step 1: State Diagram**

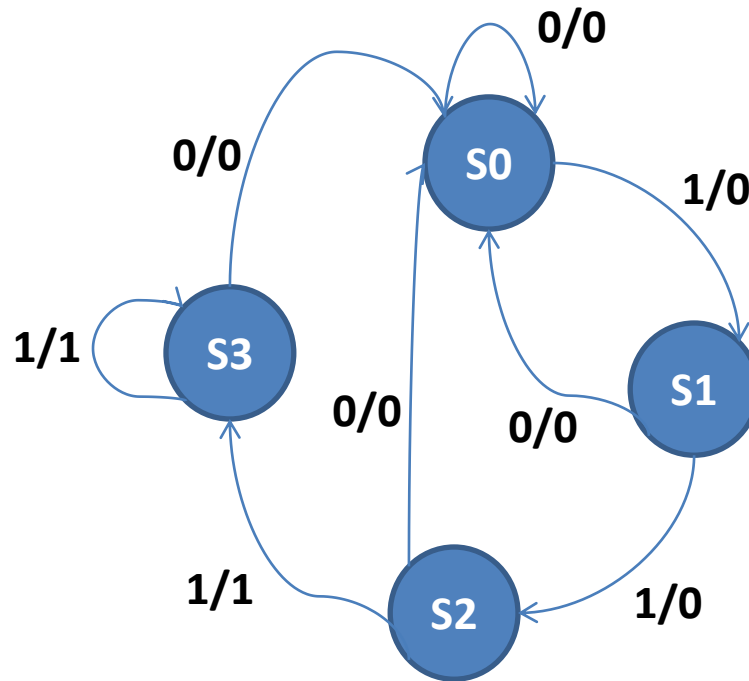

# Sequence Detector Example (Contd..)

- **Step 2: State Assignment**

$S_0 = 00$

$S_1 = 01$

$S_2 = 10$

$S_3 = 11$

# Sequence Detector Example (Contd..)

- Step 3: State Table

Present State		Input	Next State		Output
QA	QB	X	QA+	QB+	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	1

**DA = QA+**  
**DB = QB+**

# Sequence Detector Example (Contd..)

- **Step 4:** Minimized Expression


$$DA = QA_+ = (QA + QB)X$$

$$DB = QB_+ = (\overline{QB} + QA)X$$

$$Y = QAX$$

# Sequence Detector Example (Contd..)

- **Step 5: Implement Circuit**

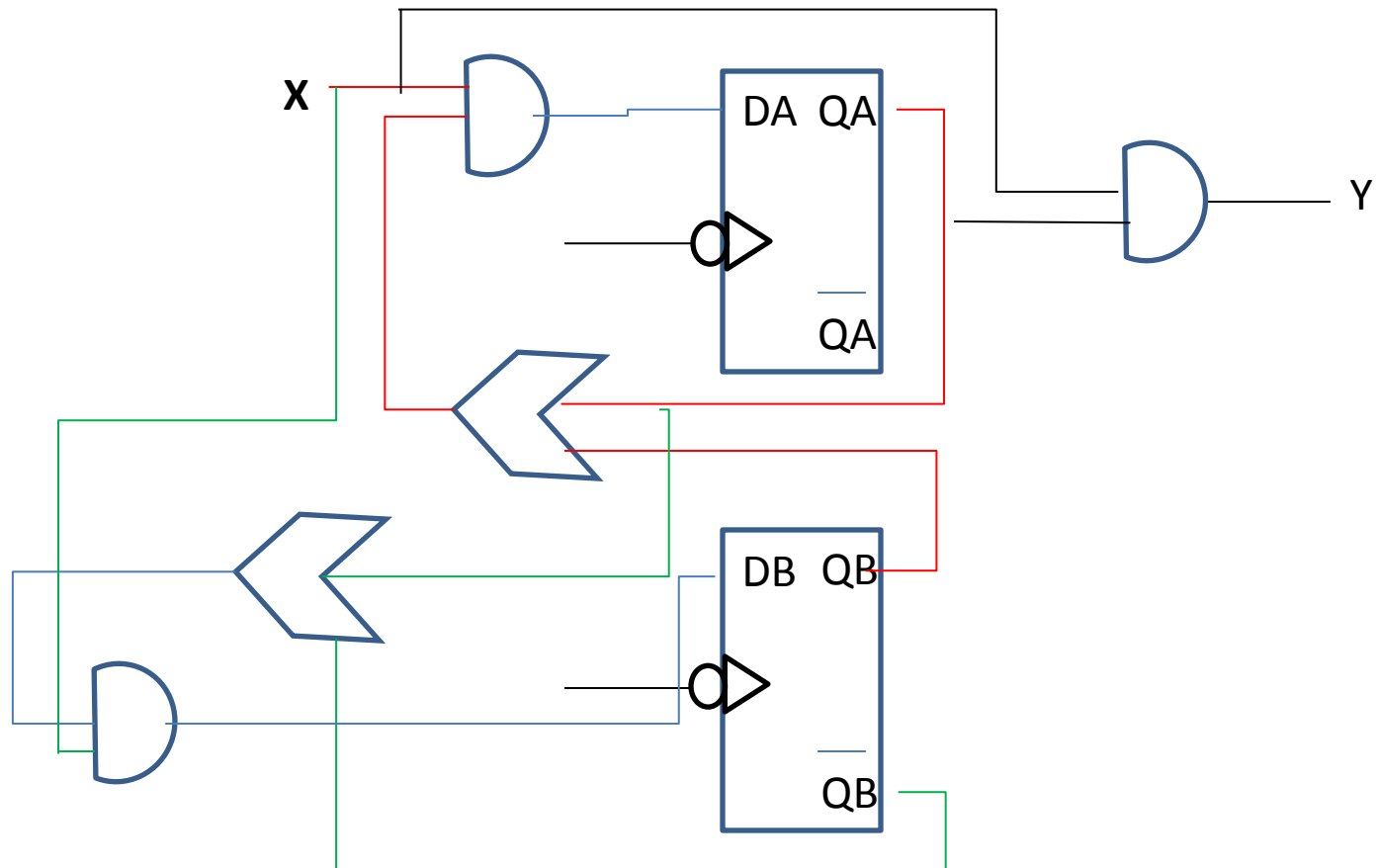

# Sequence Generator

- It is a digital logic circuit whose purpose is to produce a prescribed sequence of output
- The sequence may be of indefinite length or a predetermined fixed length
- A Binary Counter is a special type of Sequence Generator
- Sequence Generators are useful in a wide variety of coding & control applications



# Sequence Generator (Contd..)

- If you have **0101101**
- This is the sequence that you want to generate
- Then your O/P of sequence generator would be, it is going to continuously give out,  
0101101 0101101 0101101....
- So you have to decide the no. of Flip Flops

# Sequence Generator (Contd..)

- **Step 1: Number of Flip-Flops**

- J = No. of Zeros in sequence
- K = No. of Ones in sequence

$$\mathbf{N = Max (J,K)}$$

$$\mathbf{No. of FF (n) = N \leq 2^{n-1}}$$

- Now I/P sequence is **0101101**

$$J=3 \text{ \& } K=4$$

$$N = \text{Max} (J, K)$$

$$N = \text{Max} (3, 4)$$

$$\mathbf{N = 4}$$

$$\mathbf{n = 4 \leq 2^{3-1} \quad \Rightarrow \text{ if } n=3}$$

$$\mathbf{n=3}$$

# Sequence Generator (Contd..)

- **Step 2: State Table**


C	B	A	State
0	0	0	0
1	0	1	5
0	1	0	2
1	1	1	7
1	0	0	4
0	0	1	1
1	1	0	6

**Not Used Case = 3**

**So N.S. of 3 = X**

# Sequence Generator (Contd..)

- **Step 3: State Diagram**

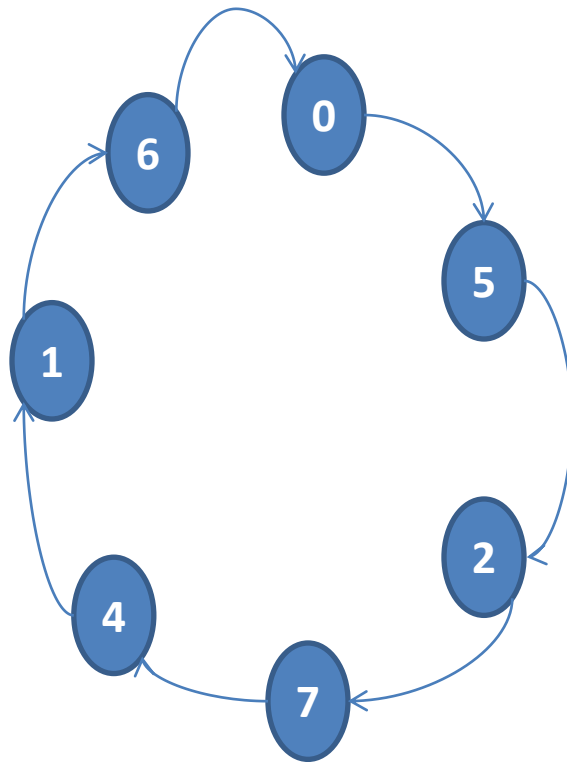

# Sequence Generator (Contd..)

- **Step 4:** Write Excitation table of JK FF

Present State	Next State	Flip – Flop Outputs	
$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

# Sequence Generator (Contd..)

- Step 5: Circuit Excitation table of JK FF

P. S.			N. S.			FF I/P					
C	B	A	C+	B+	A+	J <sub>C</sub>	K <sub>C</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
0	0	0	1	0	1	1	X	0	X	1	X
0	0	1	1	1	0	1	X	1	X	X	1
0	1	0	1	1	1	1	X	X	0	1	X
0	1	1	X	X	X	X	X	X	X	X	X
1	0	0	0	0	1	X	1	0	X	1	X
1	0	1	0	1	0	X	1	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	1	0	0	X	0	X	1	X	1

# Sequence Generator (Contd..)

- Step 6: Derive Expression

$$JC = \overline{C}$$

$$KC = \overline{A} + \overline{B}$$

$$JB = A$$

$$KB = C$$

$$JA = \overline{C} + \overline{B}$$

$$KA = A$$

# Sequence Generator (Contd..)

